

IN 221 (AUG) 3:0
Sensors and Transducers
Electromagnetic Sensors and Transducers
Lecture 3


A. Mohanty

Department of Instrumentation and Applied Physics (IAP)
Indian Institute of Science
Bangalore 560012

August 28, 2023


LVDT with fixed coils and movable core

LVDT with fixed coils and movable core

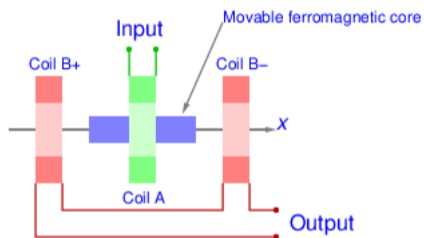

- Coils A, B₊, and B₋ are fixed.
- Fields due to B₊ and B₋ are in opposition.
- Many modern LVDTs are of this type.


Circuit for multiplication: Gilbert Cell

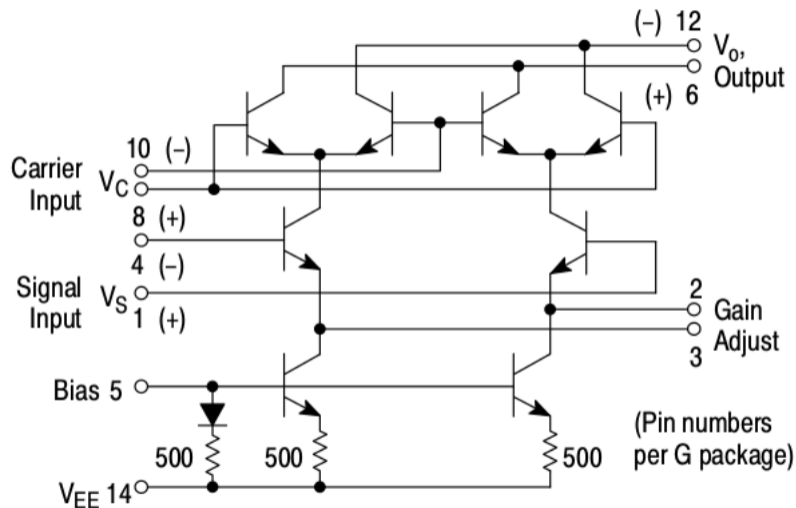

Gilbert cell used in MC1496

Circuit for multiplication: Sampling Gate


Diode Sampling Gate

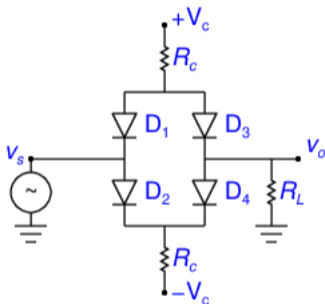

Diode sampling gate circuit: $v_o = v_s$, if V_c is able to turn the diodes on, otherwise $v_o = 0$.

If v_s and V_c are both sinusoids of the same frequency and V_c is large in amplitude, then v_o is proportional to the component of v_s along V_c .


Baxandall Oscillator

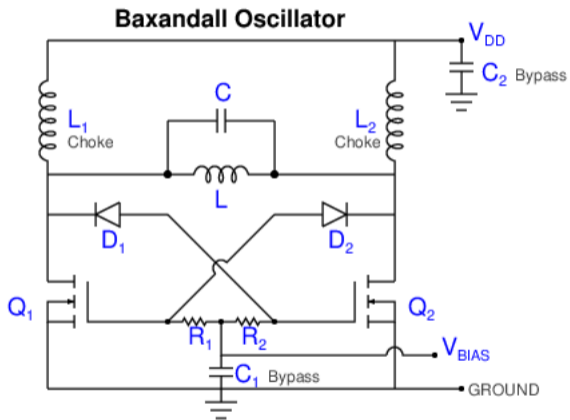


Baxandall Oscillator Parts

- Field coil $L = 97 \mu\text{H}$
- $C = 10.29 \text{ nF}$
- MOSFETs: ST55NF06L or IRF540N
- Diodes: 1N4007
- $R_1 = R_2 = 470 \Omega$
- Chokes: $L_1 = L_2 = 1 \text{ mH}$
- Bypass capacitors C_1, C_2 not used.
- $V_{\text{DD}} = V_{\text{BIAS}} = 12.0 \text{ V}$

LVDT Demo: System

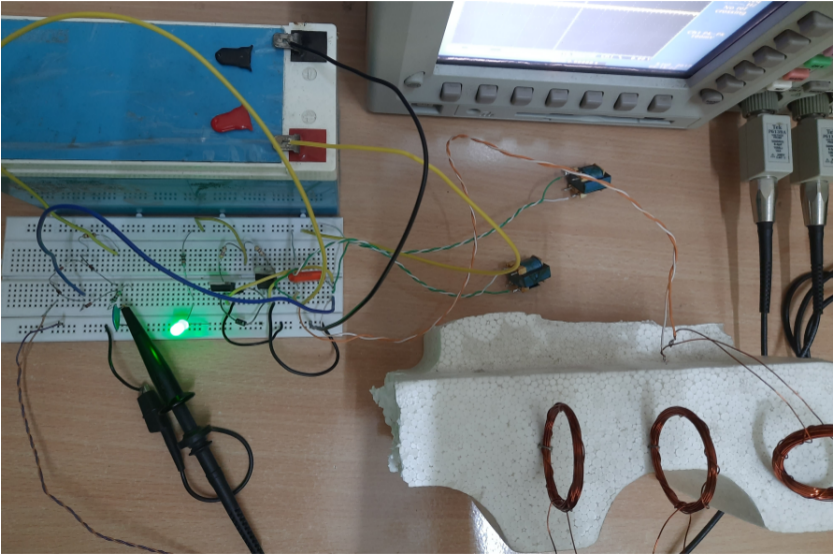


LVDT Demo: Oscillation

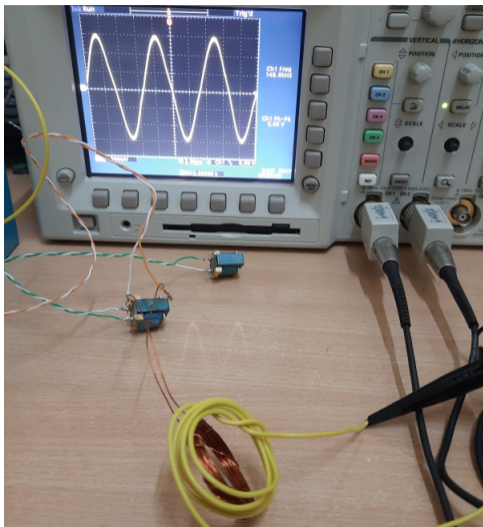


Frequency of oscillation: $f = 148.6 \text{ kHz}$.


LVDT Demo: Coil moved left

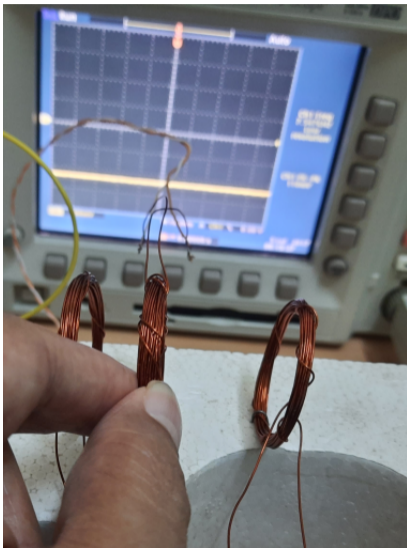

LVDT Demo: Coil close to centre

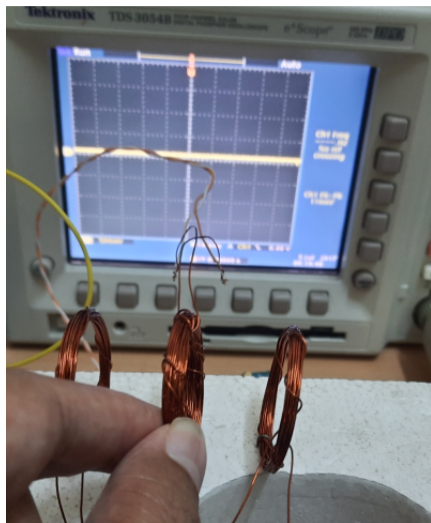

LVDT Demo: Coil moved right

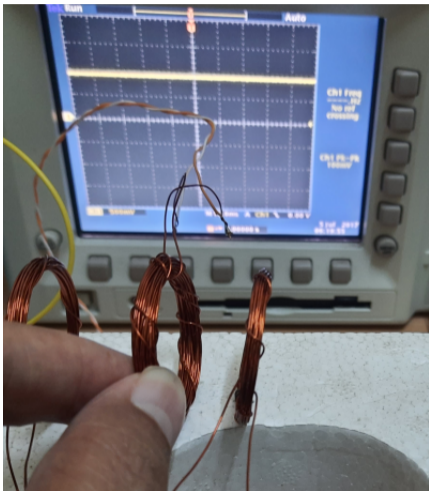

Temperature Sensors

- Thermistor
- Thermocouple
- Resistance Thermometer
- Silicon Bandgap Temperature Sensor
- Infrared Temperature Sensor

Thermistor

- Resistor whose resistance changes with temperature.
- Usually made of semiconductors.
- Change of resistance is more than that in metal resistors.
- Usually nonlinear.
- Limited range of use: $-90\text{ }^{\circ}\text{C}$ to $130\text{ }^{\circ}\text{C}$
- Two types: NTC and PTC
- NTC: Negative Temperature Coefficient, resistance decreases with increase in temperature
- PTC: Positive Temperature Coefficient, resistance increases with increase in temperature
- NTC type is more commonly used.
- Can be quite sensitive, but not as accurate as other types of temperature sensors.
- Also used to limit starting current.

Thermocouple

- Involves junctions of two different metals.
- Generates a small voltage that is roughly proportional to the temperature difference of the two junctions.
- Based on Seebeck effect
- Many types available: Types K, J, N, R, S, B, T, E, and others.
- Advantage: Wide range (from $-270\text{ }^{\circ}\text{C}$ to $1700\text{ }^{\circ}\text{C}$)
- Advantage: Requires no external power
- Disadvantage: Output is quite small, usually requires amplification
- Disadvantage: Amplification can be challenging

Resistance Thermometer

Resistance Temperature Detector (RTD)

- The resistivity of metals is a linear function of temperature over a wide range of temperatures.
- Usually a very pure form of the metal is used.
- A resistor made of the metal is enclosed in some form of protective housing.
- Commonly used metals: Platinum, Copper, Nickel
- Platinum can work till 600 °C.

Temperature Coefficient of Resistance (TCR)

Let the resistance of a resistor be R_{ref} at temperature T_{ref} and R at temperature T . Then for metal resistors over a wide range of temperatures,

$$R = R_{\text{ref}}[1 + \alpha(T - T_{\text{ref}})] \quad (1)$$

where α is called the temperature coefficient of resistance (TCR). T_{ref} is usually 20 °C.


$$\alpha = \frac{R - R_{\text{ref}}}{R_{\text{ref}}(T - T_{\text{ref}})} = \frac{\Delta R}{R_{\text{ref}}\Delta T} \quad (2)$$

Units: per °C

TCR of Commonly Used Metals


Metal	α
Platinum	$3.925 \times 10^{-3} \text{ }^{\circ}\text{C}^{-1}$
Copper	$3.9 \times 10^{-3} \text{ }^{\circ}\text{C}^{-1}$
Aluminium	$3.9 \times 10^{-3} \text{ }^{\circ}\text{C}^{-1}$
Gold	$3.4 \times 10^{-3} \text{ }^{\circ}\text{C}^{-1}$
Silver	$3.8 \times 10^{-3} \text{ }^{\circ}\text{C}^{-1}$
Tungsten	$4.5 \times 10^{-3} \text{ }^{\circ}\text{C}^{-1}$
Iron	$5.0 \times 10^{-3} \text{ }^{\circ}\text{C}^{-1}$
Nickel	$6.0 \times 10^{-3} \text{ }^{\circ}\text{C}^{-1}$
Tin	$4.5 \times 10^{-3} \text{ }^{\circ}\text{C}^{-1}$
Lead	$3.9 \times 10^{-3} \text{ }^{\circ}\text{C}^{-1}$

Two-wire Configuration

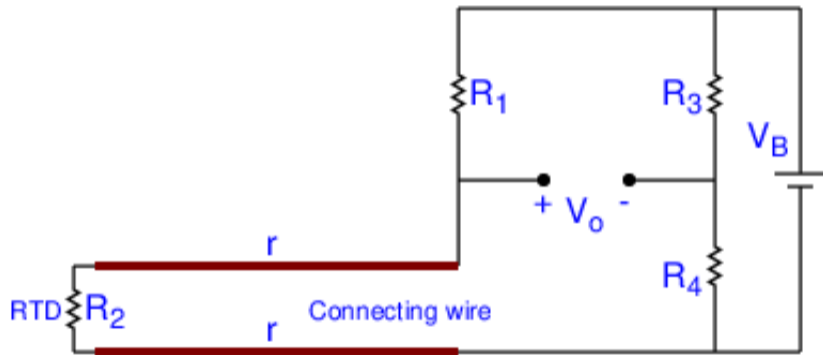

Disadvantage: r depends on the length of the connecting wire and only affects R_2 .

Three-wire Configuration

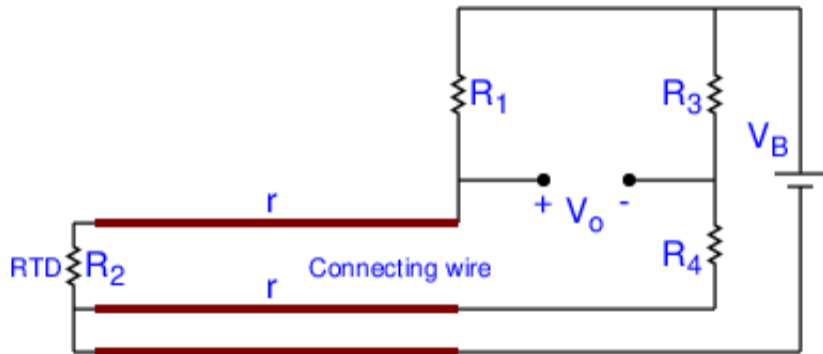

Advantage: r affects both R_2 and R_4 equally.

Silicon Bandgap Temperature Sensor

The difference in voltage drop across two identical diodes or base to emitter junctions:

$$\Delta V_{BE} = \frac{kT}{q} \ln \left(\frac{I_{C1}}{I_{C2}} \right) \quad (3)$$

Here I_{C1} and I_{C2} are the diode or the collector currents.

- Can be part of an integrated circuit
- Reasonably accurate
- Inexpensive
- Example: LM35 temperature sensor IC


Practice Problems

- 1 The electrodes of a parallel plate capacitor are circular discs, each having a radius of 10 cm. If the electrodes are separated by an air gap of 1 mm, calculate the capacitance neglecting fringing fields.
- 2 A sine wave signal having peak voltage 20 V and frequency 10 MHz is applied across a 1 nF capacitor. Calculate the peak current in the capacitor.
- 3 A circular coil has 10 turns of wire with radius 10 cm. Calculate the magnitude of B on the axis of the coil at a distance 5 cm from the centre of the loop due to a 10 A current in the coil. Assume that there are no magnetic materials near the coil.
- 4 A resistor constructed using platinum wire has resistance $100\ \Omega$ at $20\ ^\circ\text{C}$. What will be its resistance at $10\ ^\circ\text{C}$?
- 5 In the Wheatstone bridge shown on Slide 20 of Lecture 1, $V_B = 10\ \text{V}$, $R_1 = R_4 = 100\ \Omega$, and $R_2 = R_3 = 96\ \Omega$. Calculate V_0 .

Answers to Practice Problems

- ① 278.157 pF
- ② 1.256 64 A
- ③ 44.9588 μT
- ④ 96.075 Ω
- ⑤ -204.082 mV

Spring-Mass-Dashpot System: Modelling

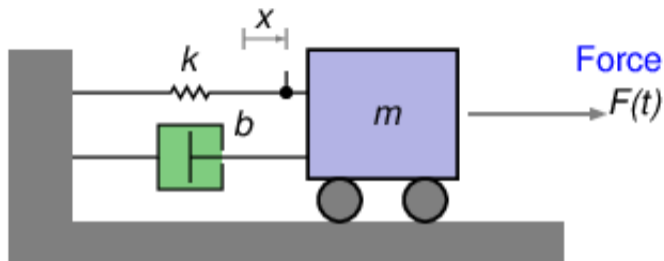

x : Displacement of the mass from its equilibrium position

$$m\ddot{x} + b\dot{x} + kx = F \quad (4)$$

F : Force

$v = \dot{x}$: Velocity

Relationship between force and velocity:

$$m\ddot{v} + b\dot{v} + kv = \dot{F} \quad (5)$$

Tension in the Dashpot

- Here the applied force $F(t)$ is the input.
- We could consider the velocity $v(t)$ as the output.
- A better choice is to consider the tension in the dashpot, $F_d(t) = bv(t)$, as the output.
- $F_d(t)$ is the force endured by the dashpot.
- Having both input and output as forces makes the mathematics neater.

Relationship between $F(t)$ and $F_d(t)$:

$$m\ddot{F}_d + b\dot{F}_d + kF_d = b\dot{F} \quad (6)$$