

IN 277 Notes 6

Comparators

Positive Feedback and Hysteresis


RC Square Wave Oscillators

A. Mohanty

Department of Instrumentation and Applied Physics
Indian Institute of Science
Bangalore 560012

October 28, 2025

Operational Amplifier as a Comparator

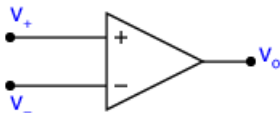



$$v_o = \begin{cases} V_{OH} & v_+ > v_-, \\ V_{OL} & v_+ < v_-. \end{cases} \quad (1)$$

Uses: Waveform shaping, Analogue to Digital Conversion, ...


Comparator

- Not all operational amplifiers are suitable for use as comparators.
- The inputs may have special diode protection making it unsuitable for use as a comparator. Example: OP07
- Comparator ICs (Example: LM339)



Positive Comparator

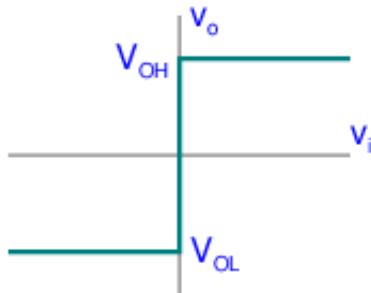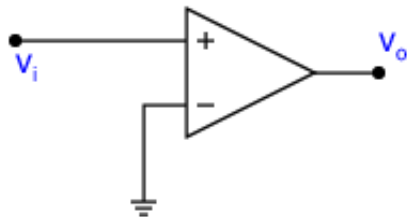



Negative Comparator

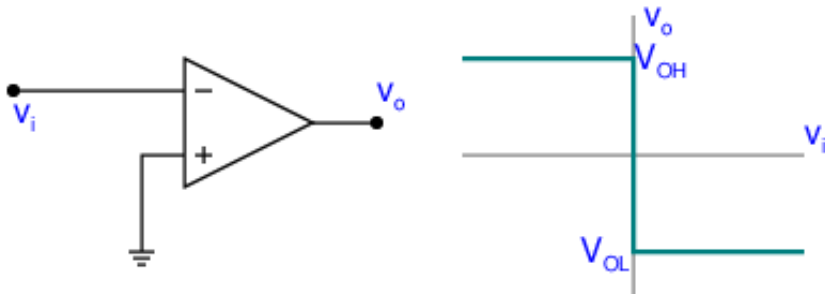


Positive Comparator with Shift

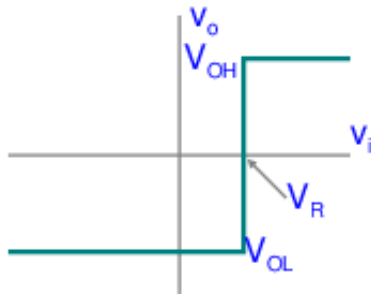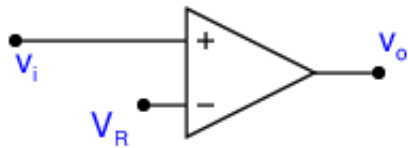

Negative Comparator with Shift

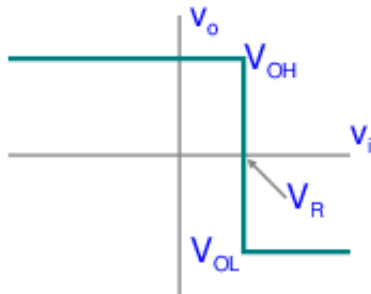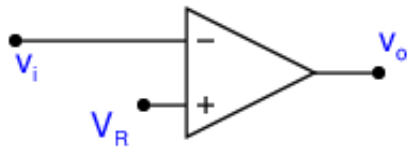

Positive Comparator with Hysteresis

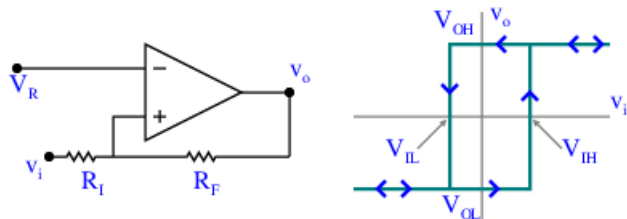

$$V_{IH} = \left(1 + \frac{R_I}{R_F}\right) V_R - \frac{R_I}{R_F} V_{OL}. \quad (2)$$

$$V_{IL} = \left(1 + \frac{R_I}{R_F}\right) V_R - \frac{R_I}{R_F} V_{OH}. \quad (3)$$

Derivation follows.

V_{IH} Formula: Positive Comparator with Hysteresis

$$v_+ = \frac{R_F}{R_F + R_I} v_i + \frac{R_I}{R_F + R_I} v_o.$$

For this value to be more than $v_- = V_R$, even when $v_o = V_{OL}$, it is required that

$$\frac{R_F}{R_F + R_I} v_i + \frac{R_I}{R_F + R_I} V_{OL} > V_R.$$

$$\Rightarrow v_i + \frac{R_F + R_I}{R_F} \frac{R_I}{R_F + R_I} V_{OL} > \frac{R_F + R_I}{R_F} V_R.$$

$$\Rightarrow v_i + \frac{R_I}{R_F} V_{OL} > (1 + R_I/R_F) V_R.$$

$$\Rightarrow v_i > (1 + R_I/R_F) V_R - \frac{R_I}{R_F} V_{OL} = V_{IH}.$$

V_{IL} Formula: Positive Comparator with Hysteresis

$$v_+ = \frac{R_F}{R_F + R_I} v_i + \frac{R_I}{R_F + R_I} v_o.$$

For this value to be less than $v_- = V_R$, even when $v_o = V_{OH}$, it is required that


$$\frac{R_F}{R_F + R_I} v_i + \frac{R_I}{R_F + R_I} V_{OH} < V_R.$$

$$\Rightarrow v_i + \frac{R_F + R_I}{R_F} \frac{R_I}{R_F + R_I} V_{OH} < \frac{R_F + R_I}{R_F} V_R.$$

$$\Rightarrow v_i + \frac{R_I}{R_F} V_{OH} < (1 + R_I/R_F) V_R.$$

$$\Rightarrow v_i < (1 + R_I/R_F) V_R - \frac{R_I}{R_F} V_{OH} = V_{IL}.$$

Negative Comparator with Hysteresis

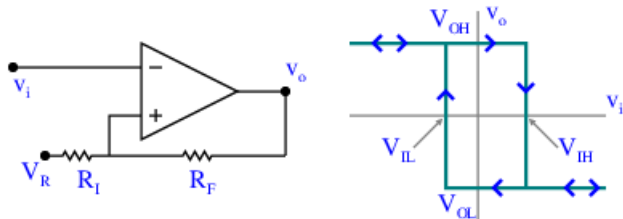

$$V_{IH} = \frac{R_F}{R_F + R_I} V_R + \frac{R_I}{R_F + R_I} V_{OH}. \quad (4)$$

$$V_{IL} = \frac{R_F}{R_F + R_I} V_R + \frac{R_I}{R_F + R_I} V_{OL}. \quad (5)$$

Derivation follows.

Derivation: Negative Comparator with Hysteresis

$$v_+ = \frac{R_F}{R_F + R_I} V_R + \frac{R_I}{R_F + R_I} v_o.$$

For $v_i = v_-$ to be more than v_+ , even when $v_o = V_{OH}$, it is required that

$$v_i > \frac{R_F}{R_F + R_I} V_R + \frac{R_I}{R_F + R_I} V_{OH} = V_{IH}.$$


For $v_i = v_-$ to be less than v_+ , even when $v_o = V_{OL}$, it is required that

$$v_i < \frac{R_F}{R_F + R_I} V_R + \frac{R_I}{R_F + R_I} V_{OL} = V_{IL}.$$

Uses of Comparators with Hysteresis

- Noise immunity
- Many line receiver ICs such as MC 1489 have built-in hysteresis to combat noise.
- Oscillators

Oscillator A

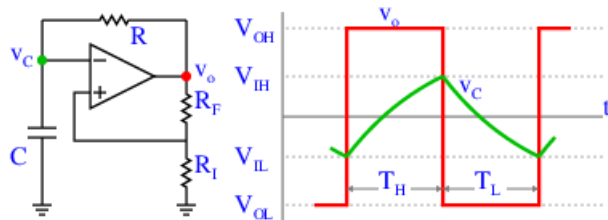


$$T_H = RC \ln \frac{V_{OH} - V_{IL}}{V_{OH} - V_{IH}}. \quad (6)$$

$$T_L = RC \ln \frac{V_{IH} - V_{OL}}{V_{IL} - V_{OL}}. \quad (7)$$


Here, $V_{IH} = \frac{R_I}{R_F + R_I} V_{OH}$, and $V_{IL} = \frac{R_I}{R_F + R_I} V_{OL}$. These were obtained by setting $V_R = 0$ in the expressions given for the negative comparator with hysteresis.

Implementation: Oscillator A

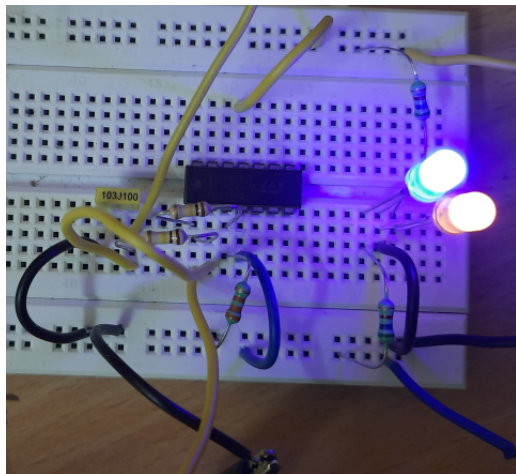


Uses $R_F = 100\text{ k}\Omega$, $R_I = 33\text{ k}\Omega$, $R = 100\text{ k}\Omega$, and $C = 10\text{ nF}$.
IC: TL084, Supply: $\pm 12\text{ V}$.

Output: Oscillator A

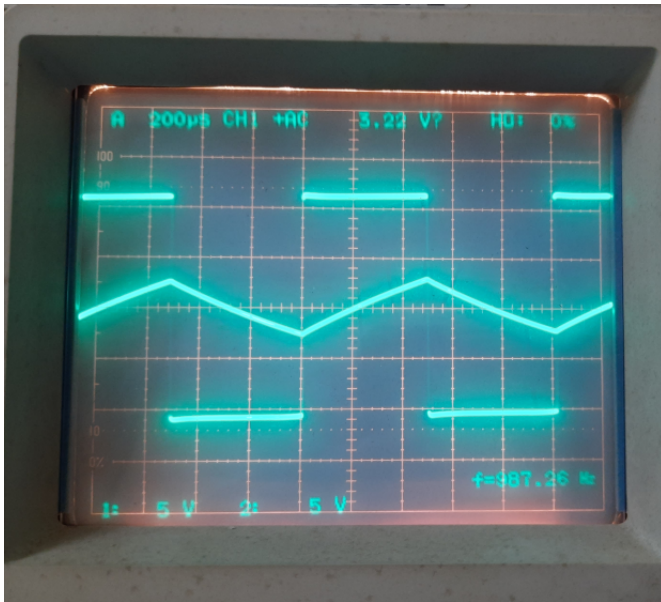

Oscillator B

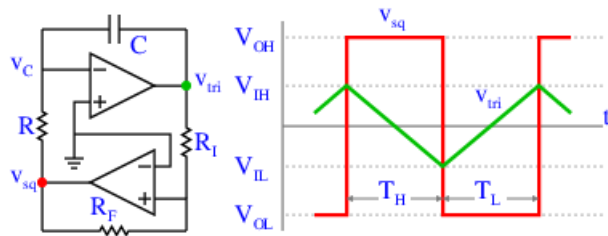


$$T_H = RC \frac{V_{IH} - V_{IL}}{V_{OH}}. \quad (8)$$

$$T_L = RC \frac{V_{IH} - V_{IL}}{-V_{OL}}. \quad (9)$$

Here, $V_{IH} = -\frac{R_I}{R_F} V_{OL}$, and $V_{IL} = -\frac{R_I}{R_F} V_{OH}$. These were obtained by setting $V_R = 0$ in the expressions given for the positive comparator with hysteresis.


This oscillator has both square wave and triangle wave outputs.

Implementation: Oscillator B

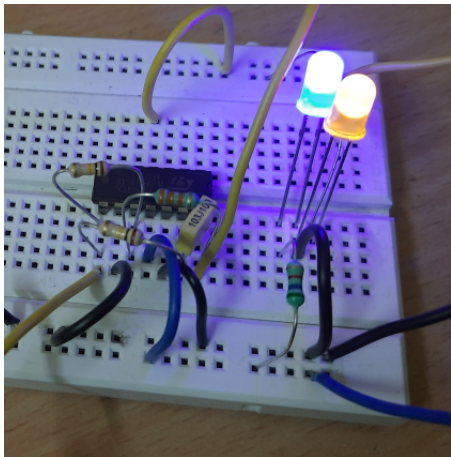

Uses $R_F = 100\text{ k}\Omega$, $R_I = 33\text{ k}\Omega$, $R = 100\text{ k}\Omega$, and $C = 10\text{ nF}$.
IC: TL084, Supply: $\pm 12\text{ V}$.

Output: Oscillator B

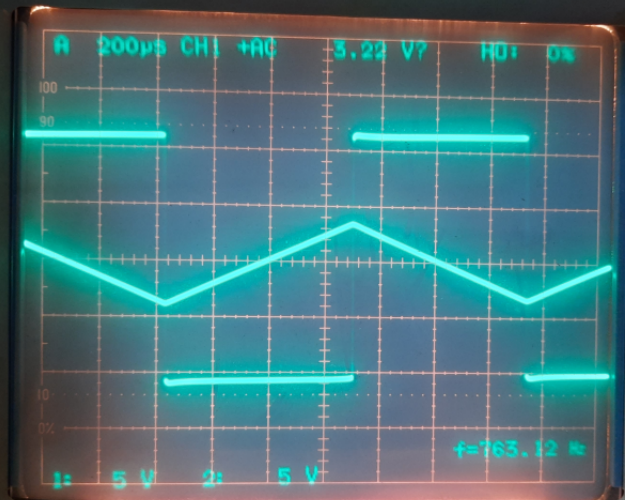


Schmitt Trigger Inverter

- Logic inverter designed to have hysteresis
- Improves noise immunity
- Frequently used in interfacing
- Examples: 74LS14, 74HC14, 74HCT14
- Can be used for making an RC oscillator
- Similar to Oscillator A

Symbol: Schmitt Trigger Inverter



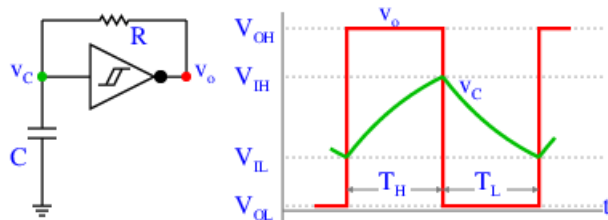RC Oscillator using an inverting Schmitt Trigger




$$T_H = RC \ln \frac{V_{OH} - V_{IL}}{V_{OH} - V_{IH}}. \quad (10)$$

$$T_L = RC \ln \frac{V_{IH} - V_{OL}}{V_{IL} - V_{OL}}. \quad (11)$$

V_{OH} , V_{OL} , V_{IH} , and V_{IL} are to be obtained from IC data sheet or measured.
For CMOS gates, $V_{OH} = V_{DD}$, $V_{OL} = 0$.


Many oscillators used in digital systems are of this type.

Implementation: 74HC14 RC Oscillator

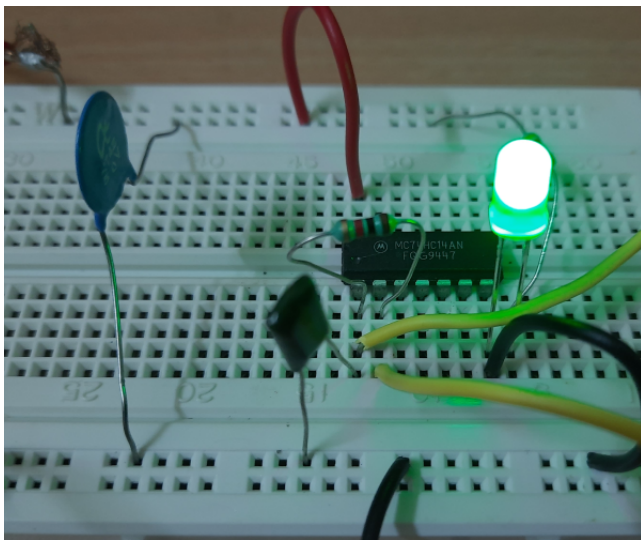

Uses $R = 1\text{ k}\Omega$, and $C = 6.8\text{ nF}$.

Output: 74HC14 RC Oscillator

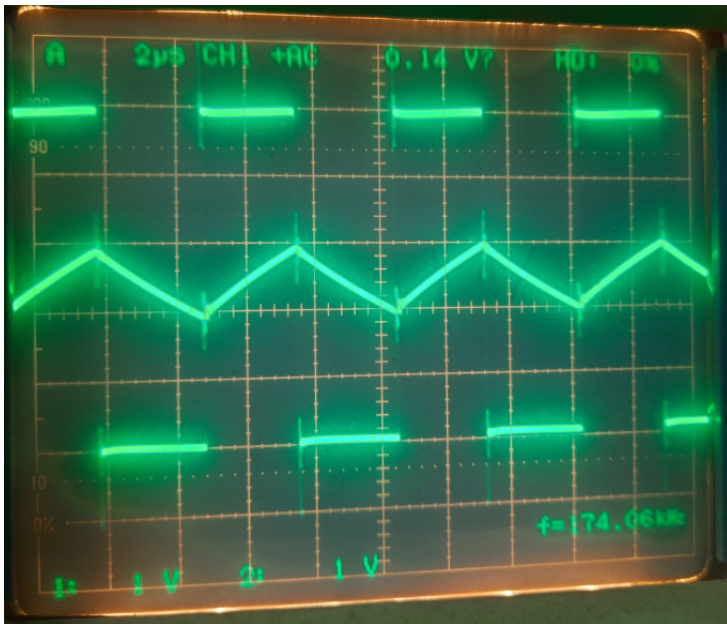

Calculation: 74HC14 RC Oscillator

From the output display, $V_{OH} = 5\text{ V}$, $V_{OL} = 0\text{ V}$, $V_{IH} = 3\text{ V}$, $V_{IL} = 2\text{ V}$.

Using $R = 1\text{ k}\Omega$, and $C = 6.8\text{ nF}$ we get $T_H = 2.7572\text{ }\mu\text{s}$, and $T_L = 2.7572\text{ }\mu\text{s}$.

Calculated period $T = T_H + T_L = 5.5143\text{ }\mu\text{s}$.

Calculated frequency $f = 1/T = 181.35\text{ kHz}$.

The measured frequency (as seen on the screen) is 174.06 kHz .